

Carlos Gross-Martinez

CDA3201C

Logic Design Course

Lab 4: Tracing Master Slave and Waltz Counter

JK Flip-Flops Timing Diagram Trace

• CDA3201 • Intro to Logic Design •


Lab Assignment

4


Name: Carlos Gross-Martinez

Grade: /100

 4) [40] Consider the following sequential circuit with two positive-edge-triggered JK flip-flops.



 4.a) [4] Trace the timing diagram for the above circuit by hand.



Logic Drawing JK Flip-Flops Using Logic Chips

• CDA3201 • Intro to Logic Design •


Lab Assignment

4

Name: Carlos Gross-Martinez


Grade: /100

 - 4.c) [8] Verify the circuit design/behavior by implementing the circuit using Quartus and the CD4027BE J-K Flip Flop. Review the PowerPoint in this section know how set the value of CLR and X to a value within a time period. SET1 and SET2 are active high so disable them by connecting permanently to low so see how to set a constant (0) throughout the time period, and how to set the fluctuating value of the clock. Turn in a picture of your Schematic and a picture of the VectorWaveForm generated to match the given timing diagram



 - 4.b) [16] Build the above circuit using the CD4027BE dual JK flip-flop logic chip on your breadboard and then connect it to your test platform to test it. Use the chip block diagram below to plan for your wiring. Use 2 logic switches for inputs X and CLR (Reset), and one pulse switch for the Clock. Use 4 LEDs to observe $X=J1=K1$, $Q1=J2=K2^*$, $Q2$, and $Z=Q1^*+Q2^*$. Tie the SET inputs to low as they are active high. Plan your circuit below.

Observation: If X is kept high, Q1 will toggle at every positive Clock transition because $J1=K1=X=1$ (toggle mode).



JK Flip-Flops and Waltz Counter State Diagram and Boolean expression Simplification

• CDA3201 • Intro to Logic Design •

4

Name: Carlos Gross-Martinez
Grade: /100

4.d) [12] From the analysis of the circuit above, draw the State Table and the State Diagram.

State Diagram:

Present State	Input	Output	Next State	Flip Flop Transition
State	Q_2 Q_1	Z	Q_2^+ Q_1^+	J_2 K_2 J_1 K_1
A	0 0	1	0 0	0 x 0 x
B	0 1	1	0 1	0 x 0 x
C	1 0	1	1 0	x 0 x 0
D	1 1	0	1 1	x 0 x 0

4.e) [60] Build a "Waltz Counter", the Waltz is a dance where you keep time by counting 1, 2, 3, 1, 2, 3, 1, 2, 3, 1...

[10] Draw the State Diagram and Table

State Diagram:

Present State	Input	Output	Next State	Flip Flop Transition
State	Q_2 Q_1	Z	Q_2^+ Q_1^+	J_2 K_2 J_1 K_1
A	0 0	1	0 1	0 x 1 x
B	0 1	1	1 0	1 x x 1
C	1 0	1	1 1	x 1 0 x
D	1 1	0	0 0	x x x x

[10] Figure out the simplest Boolean Algebra Expression for 2 Output bits Z_2 and Z_1

Z_2

$Z_2 = Q_1 + Q_2$

Z_1

$Z_1 = Q_1$

[10] Figure out the simplest Boolean Algebra Expression for JK Flip Flop Inputs J_2 K_2 and J_1 K_1

J_2

$J_2 = Q_1$

K_2

$K_2 = 1$


J_1

$J_1 = Q_2$

K_1

$K_1 = 1$

Logic Drawing Waltz Counter Using Logic Chips

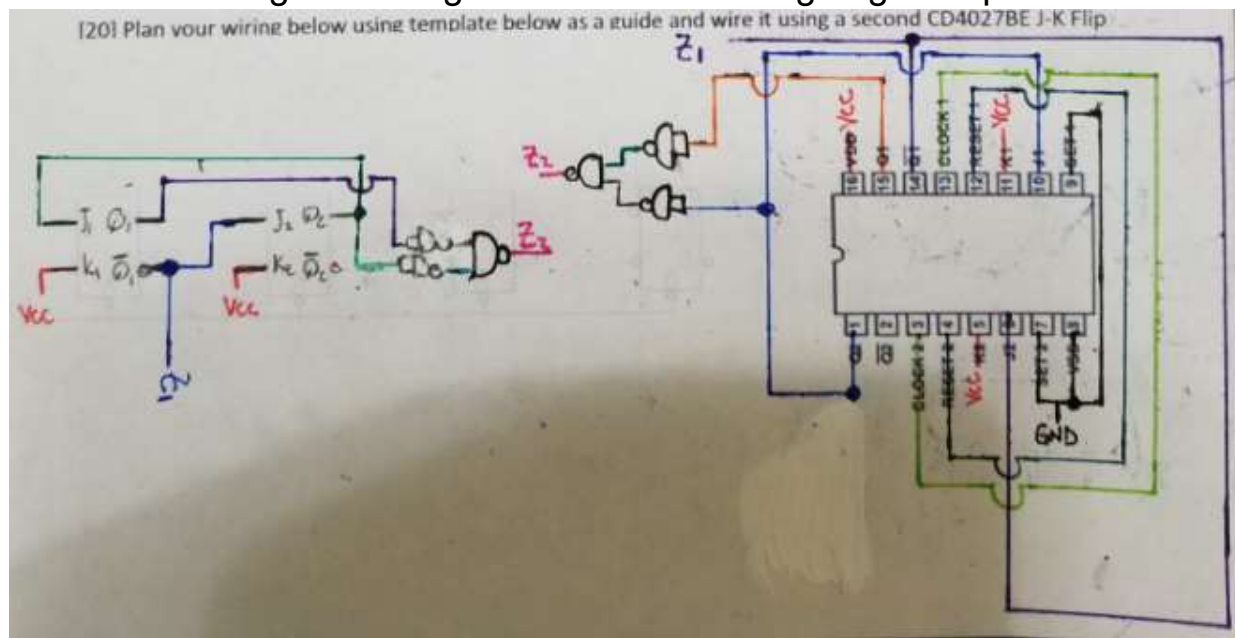

Quartus II - C:/Users/Carlos Gross/Desktop/Fall2019/LogicDesign/Lab4/Lab4_CounterTracingMasterSlaveVaiZCounter_Petrie_Gross-Martinez - Lab4_Count

File Edit View Project Assignments Processing Tools Window Help

Lab4_CounterTracingMasterSlaveVaiZCounter_Petrie_Gross-Martinez.bdf

Project Navigator

Entity	Combinational ALUTs	ALUTs	Dedicated
Stratix II: AUTO			
Lab... 6 (1)		3 (0)	5 (0)

Tasks

Row: Compilation

Task List


- Compile Design
- Analysis & Synthesis
- Edit Settings
- View Report
- Analysis & Elaboration
- Partition Merge
- Netlist Viewers
- Design Assistant (Post-Mapping)
- I/O Assignment Analysis
- Early Timing Estimate
- Filter (Place & Route)
- Assembler (Generate programming files)
- Classic Timing Analysis
- EDA Netlist Writer

Lab4_CounterTracingMasterSlaveVaiZCounter_Petrie_Gross-Martinez.bdf

Carlos Gross-Martinez
CDA3201C
Dr. Maria Larrondo Petrie
Lab 4 Counter Tracing Master Slave

Quartus Waveform Compilation Result

JK Flip-Flops and Waltz Counter

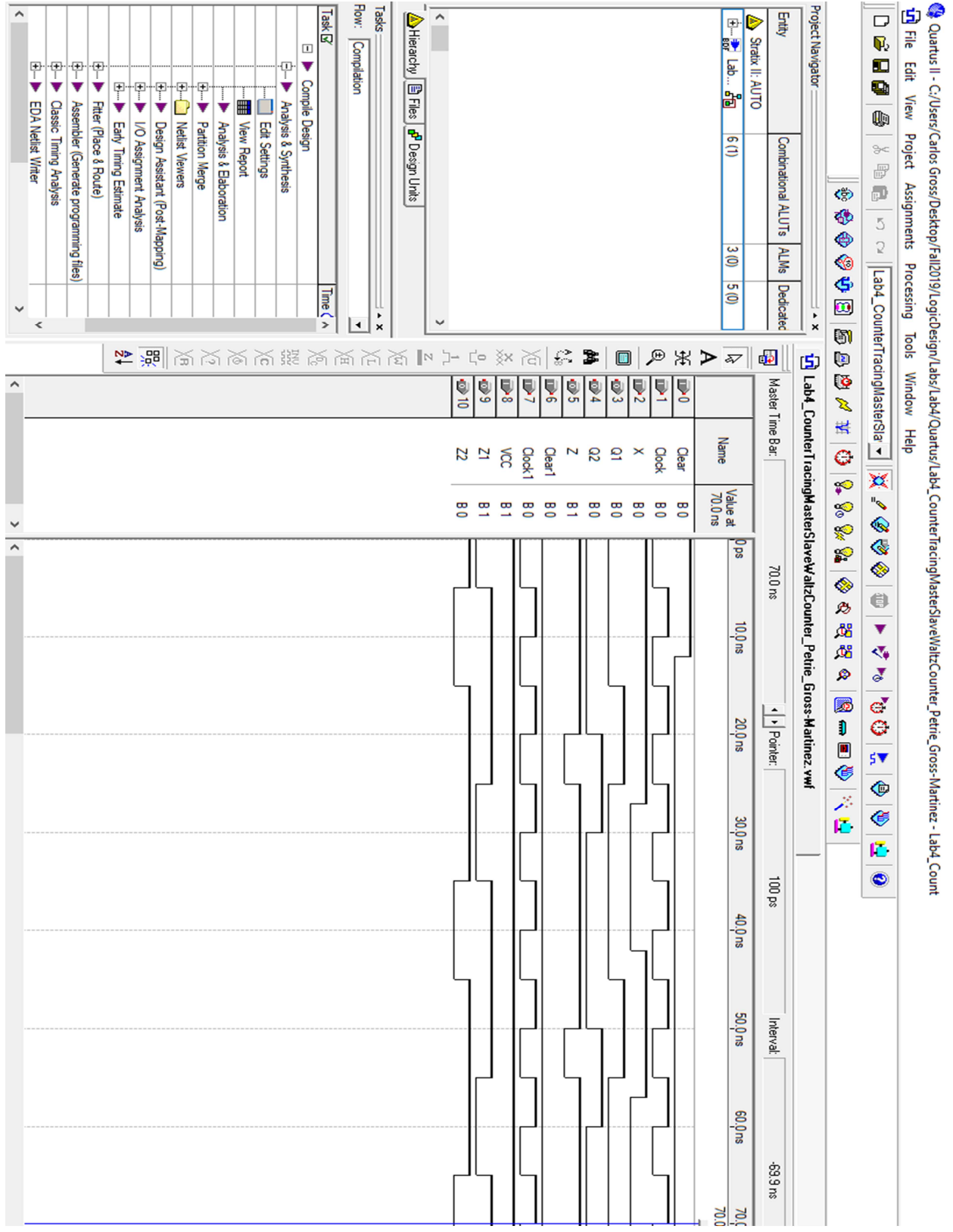

Picture of Completed Circuit on Breadboard

