


Carlos Gross-Martinez

CDA3201C

Logic Design Course

Lab 6: Dual Counter

## Dual Counter Schematic General

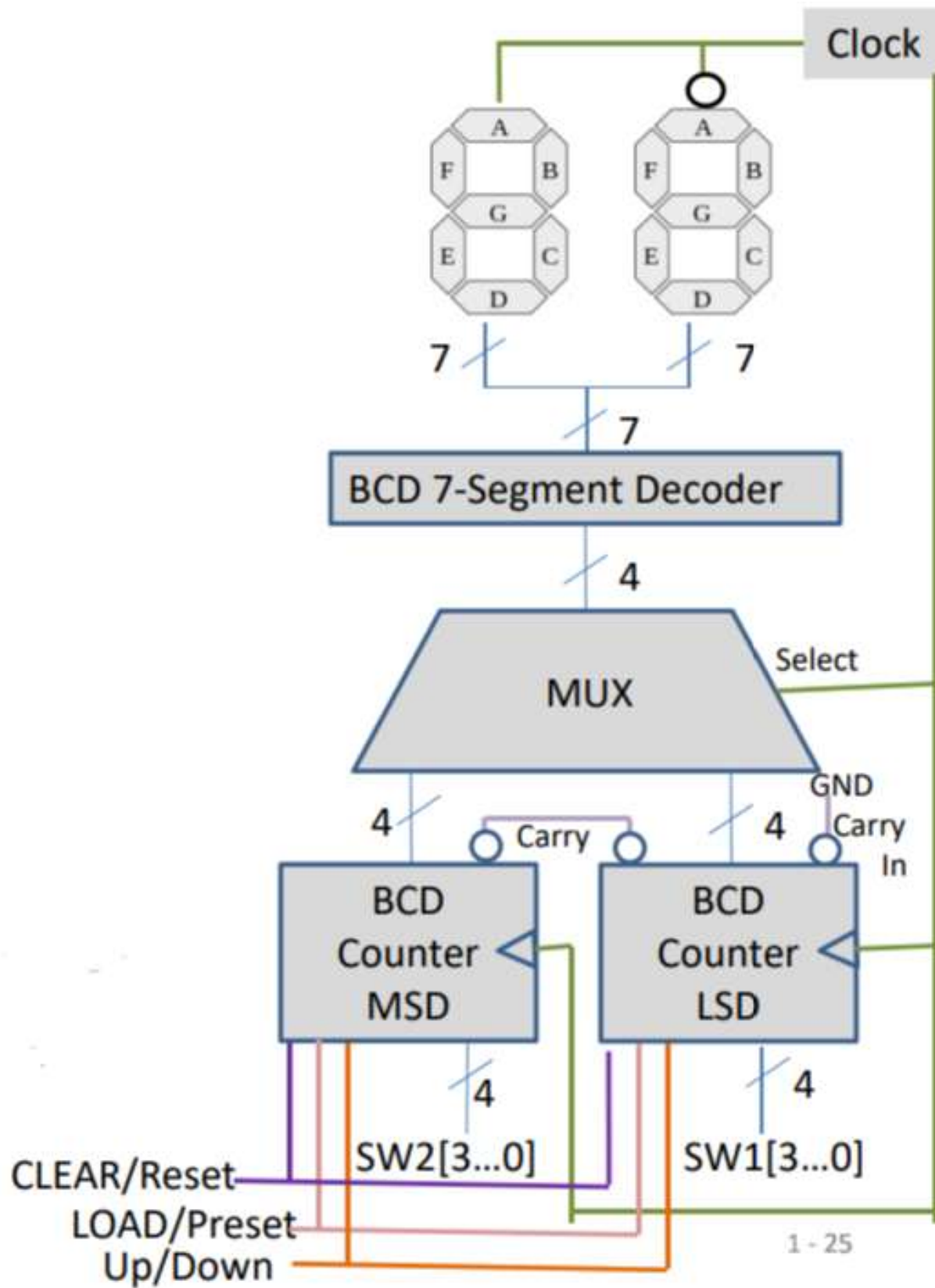

**Hints:**

- "A1...4" is the Ones digit and use the right switch bank.
- Test the display wiring by connecting the 4543 to the dip switch first.
- Use the 1 meg Ohm resistor to test you square wave signal.
- Then change it to a 100k ohm or lower.
- The "DP" is unused
- Display Connect Common1 to EITHER Common1 or Common2.

**Hint: --->**

**Common Cathode Display**  
See Hint #6

**7 Segment Display Driver**  
Build the display first!  
Then test by wiring these  
to your dip switches.  
See 4543 data sheet for pin 1,6,7  
OR Use the Hexadecimal Display

**Try different Resistor values for "R".  
What happens to the display??**

**For Lab 6**  
 $R = 1M$ : -6Hz oscillator  
 $R = 100k$ : -60Hz oscillator  
 $R = 10k$ : -600Hz oscillator

**LAB 6: 00-99 Counter**  
**Show: The Starting point**

By Perry Weinthal, FAU, Engineering, CEES Lab Manager

Sheet / File: Lab 6 -- 0to99 counter w\_generic\_display-0410 20180417.sch

Title: Logic Lab 06 -- 00 to 99 Counter

Size: A Date: Rev: 1.6 Id: 1/1

**All unused chip inputs must be connected  
To either High or Low  
-- Never leave them unattended**

**LAB 6: 00-99 Counter**  
**Shown: The Starting point**

**By Perry Weinthal, FAU, Engineering, CEECS Lab Manager**

File: Lab 6 -- O1099 counter w\_generic display-0410 20180417.sch

Title: Logic Lab 06 - 00 to 99 Counter


Size: A Date:

KICad E.D.A. eschema 4.0.2-stable

Rev: 1.6

Id: 1/1

# Dual Counter Logic Drawing

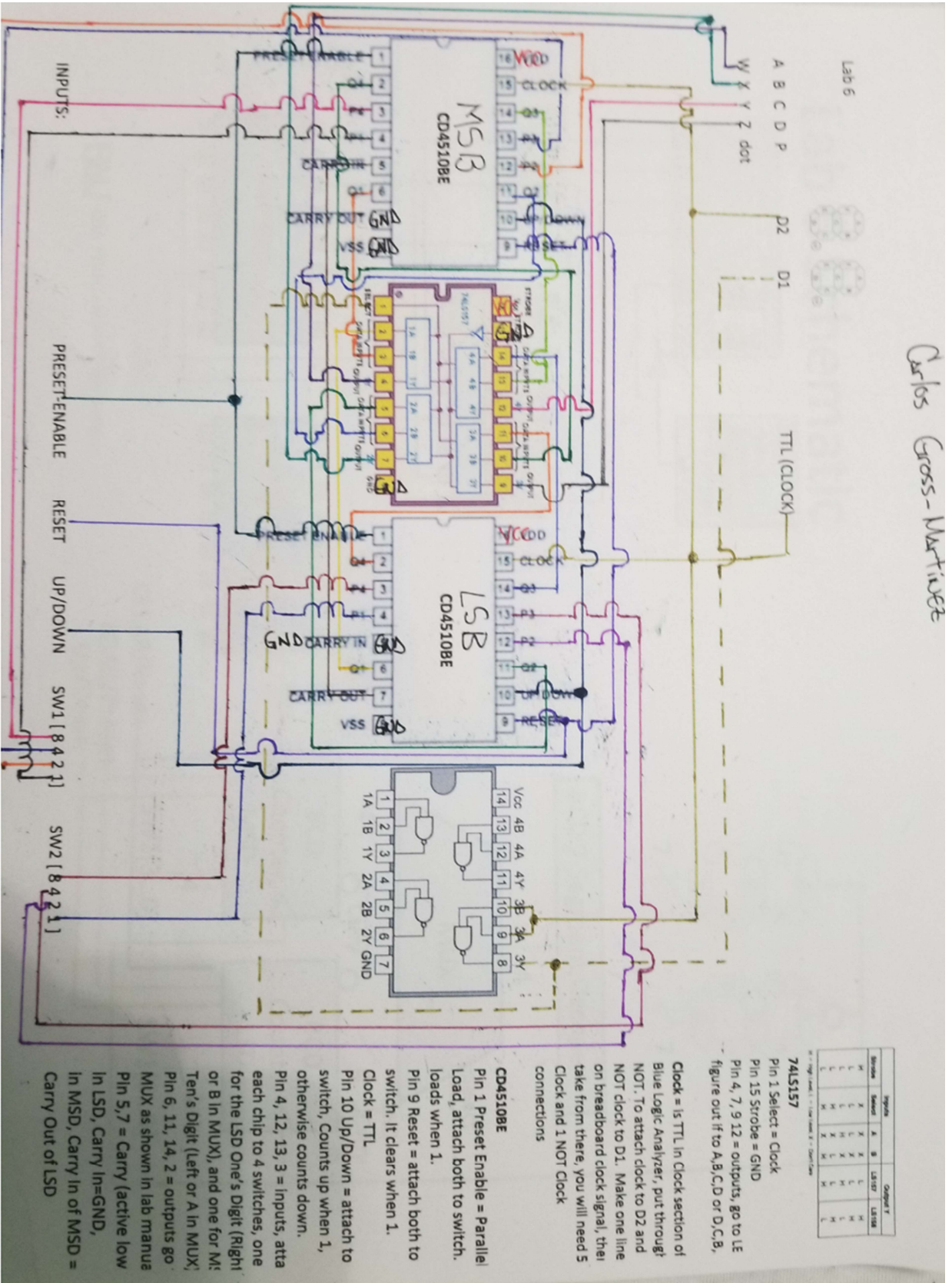



Picture of Completed Circuit on Breadboard

